

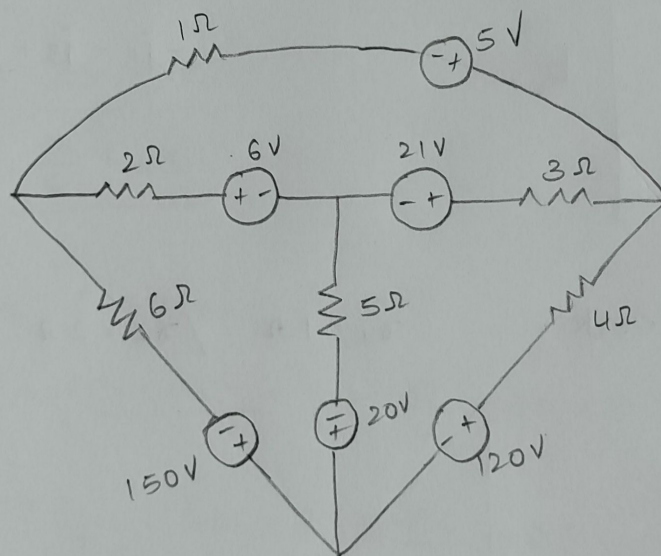
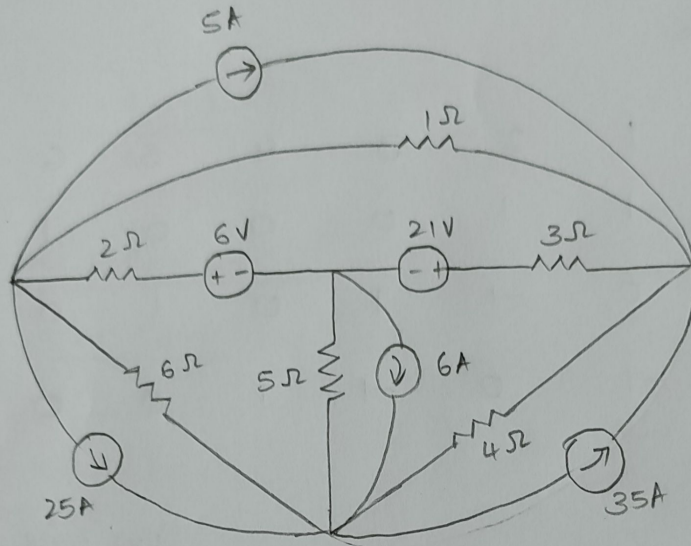




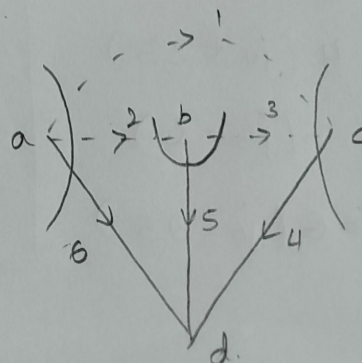
1. For the circuit shown in figure, the ohmic values also represent the branch currents. Form a tree using 4Ω , 5Ω , 6Ω branches find the branch currents using cut set matrix



OG

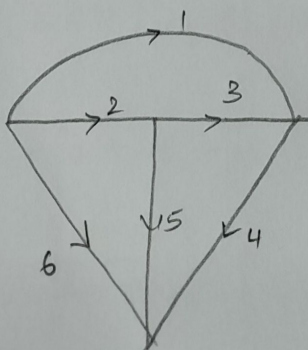

Tree

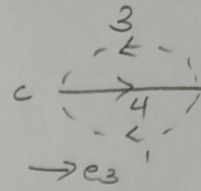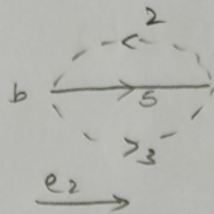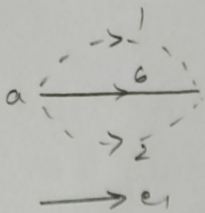

cutset schedule.

	1	2	3	4	5	6
$e_1(1,2,6)$	1	1	0	0	0	1
$e_2(2,3,5)$	0	-1	1	0	1	0
$e_3(1,3,4)$	-1	0	-1	1	0	0

column wise

$$\left. \begin{aligned} v_1 &= e_1 - e_3 \\ v_2 &= e_1 - e_2 \\ v_3 &= e_2 - e_3 \\ v_4 &= e_3 \\ v_5 &= e_2 \\ v_6 &= e_1 \end{aligned} \right\} b$$

Row wise

$$\left. \begin{aligned} j_1 + j_2 + j_6 &= 0 \\ -j_2 + j_3 + j_5 &= 0 \\ -j_1 - j_3 + j_4 &= 0 \end{aligned} \right\} a$$

from the network,

$$r_1 = 1\Omega \quad / \quad r_2 = 2\Omega \quad / \quad r_3 = 3\Omega$$

$$\left. \begin{aligned} v_1 &= j_1 - 5 \\ v_2 &= 2j_2 + 6 \\ v_3 &= 3j_3 - 21 \\ v_4 &= 4(j_4 + 33) \\ v_5 &= 5(j_5 - 6) \\ v_6 &= 6(j_6 - 25) \end{aligned} \right\} c$$

substitute c in a ,

$$v_1 = j_1 - 5$$

$$j_1 = v_1 + 5$$

$$j_1 = e_1 - e_3 + 5$$

$$2j_2 + 6 = e_1 - e_3$$

$$j_2 = \frac{e_1 - e_2 - 6}{2}$$

$$3j_3 - 21 = e_2 - e_3$$

$$j_3 = \frac{e_2 - e_3 + 21}{3}$$

$$4(j_4 + 35) = e_3$$

$$j_4 = \frac{e_3}{4} - 35$$

$$j_5 = \frac{e_2}{5} + 6$$

$$6(j_6 - 25) = e_1$$

$$j_6 = \frac{e_1}{6} + 25$$

sub for j terms in (a)

$$e_1 - e_3 + 5 + \left(\frac{e_1 - e_2 - 6}{2} \right) + \frac{e_1}{6} + 25 = 0$$

$$e_1 - e_3 + 5 + \frac{e_1}{2} - \frac{e_2}{2} - 3 + \frac{e_1}{6} + 25 = 0$$

$$e_1(1.67) - e_2(0.5) - e_3 = -22 \rightarrow (1)$$

$$-j_2 + j_3 + j_5 = 0$$

$$-\left(\frac{e_1 - e_2 - 6}{2} \right) + \frac{e_2 - e_3 + 21}{3} + \frac{e_2}{5} + 6 = 0$$

$$-e_1(0.5) + e_2(1.033) - e_3(0.33) = -16 \rightarrow \textcircled{2}$$

$$-j_1 - j_3 + j_4 = 0$$

$$-(e_1 - e_3 + 5) - \left(\frac{e_2 - e_3 + 21}{3} \right) + \left(\frac{e_3}{4} - 35 \right) = 0$$

$$-e_1 - e_2(0.33) + e_3(1.583) = 47 \rightarrow \textcircled{3}$$

solving 1, 2 and 3,

$$e_1 = -3.537 \text{ V}$$

$$e_2 = -8.957 \text{ V}$$

$$e_3 = 25.57 \text{ V}$$

$$j_1 = -24.11 \text{ A}$$

$$j_2 = -0.26 \text{ A}$$







$$j_3 = -4.53 \text{ A}$$

$$j_4 = -28.62 \text{ A}$$

$$j_5 = 4.18 \text{ A}$$

$$j_6 = 24.4 \text{ A}$$

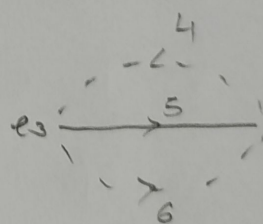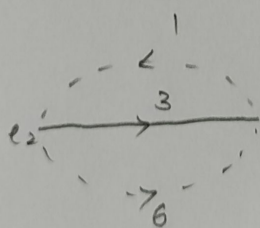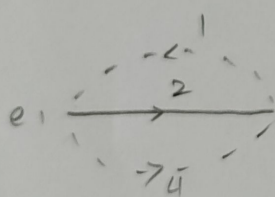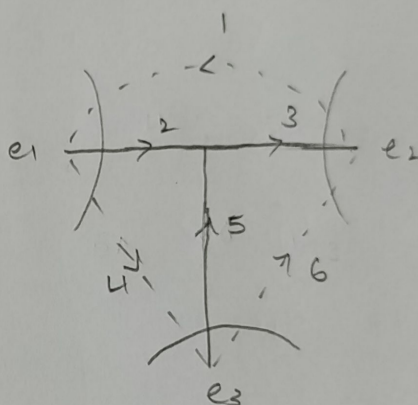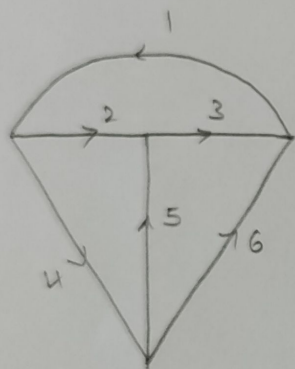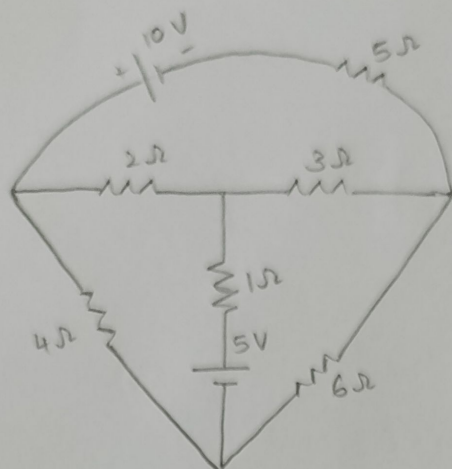2. Draw the oriented graph of a network shown in figure. Select a tree, write the cutset schedule and obtain equilibrium equation.



	1	2	3	4	5	6
$e_1(1, 2, 4)$	-1	0	0	1	0	0
$e_2(1, 3, 6)$	1	0	-1	0	0	-1
$e_3(4, 5, 6)$	0	0	0	-1	1	1

$$\left. \begin{aligned} -j_1 + j_2 + j_4 &= 0 \\ j_1 - j_3 - j_6 &= 0 \\ -j_4 + j_5 + j_6 &= 0 \end{aligned} \right\} \text{(a) Row wise}$$

Column wise,

$$\left. \begin{aligned} V_1 &= -e_1 + e_2 \\ V_2 &= e_1 \\ V_3 &= -e_2 \\ V_4 &= e_1 - e_3 \\ V_5 &= e_3 \\ V_6 &= -e_2 + e_3 \end{aligned} \right\} \text{(b)}$$

from the circuit,

$$\left. \begin{aligned} V_1 &= 5j_1 - 10 \\ V_2 &= 2j_2 \\ V_3 &= 3j_3 \\ V_4 &= 4j_4 \\ V_5 &= j_5 - 5 \\ V_6 &= 6j_6 \end{aligned} \right\} \text{(c)}$$

substitute c in b

$$j_1 = \frac{-e_1 + e_2 + 10}{5}$$

$$j_2 = \frac{e_1}{2}$$

$$j_3 = \frac{-e_2}{3}$$

$$j_4 = \frac{e_1 - e_3}{4}$$

$$j_5 = e_3 + 5$$

$$j_6 = \frac{-e_2 + e_3}{6}$$

substitute j in terms in (a)

$$-j_1 + j_2 + j_4 = 0$$

$$\frac{e_1 - e_2 + 10}{5} + \frac{e_1}{2} + \frac{e_1 - e_3}{4} = 0$$

$$0.95e_1 - 0.2e_2 - 0.25e_3 = -2 \rightarrow \textcircled{1}$$

$$j_1 - j_3 - j_6 = 0$$

$$\frac{-e_1 + e_2 + 10}{5} + \frac{e_2}{3} + \frac{e_2 - e_3}{6} = 0$$

$$-0.2e_1 + 0.7e_2 - 0.166e_3 = -2 \rightarrow \textcircled{2}$$

$$-j_4 + j_5 + j_6 = 0$$

$$\frac{-e_1 + e_3}{4} + e_3 + 5 - \frac{e_2 + e_3}{6} = 0$$

$$-0.25e_1 - 0.166e_2 + 1.416e_3 = -5 \rightarrow \textcircled{3}$$

solving 1, 2, 3,

$$e_1 = 0.287 \text{ V}$$

$$v_1 = -3.987 \text{ V}$$

$$j_1 = 1.202 \text{ A}$$

$$e_2 = -3.7 \text{ V}$$

$$v_2 = 0.287 \text{ V}$$

$$j_2 = 0.1435 \text{ A}$$

$$e_3 = -3.93 \text{ V}$$

$$v_3 = 3.7 \text{ V}$$

$$j_3 = 1.85 \text{ A}$$

$$v_4 = 4.217 \text{ V}$$

$$j_4 = 1.05 \text{ A}$$



$$v_5 = -3.93 \text{ V}$$

$$j_5 = 1.07 \text{ A}$$





$$v_6 = -0.23 \text{ V}$$

$$j_6 = 0.038 \text{ A}$$

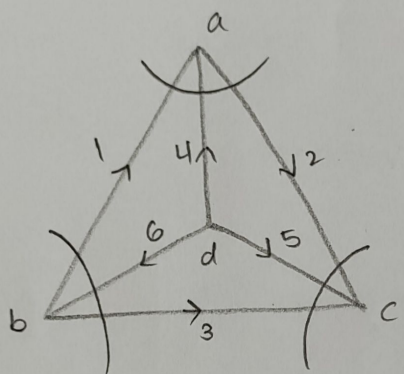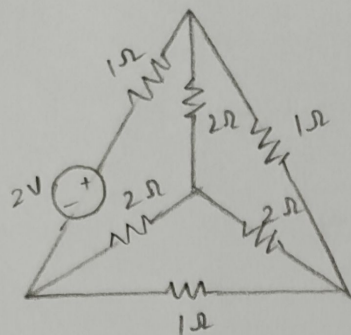3. For this network shown in Figure, write down the cutset matrix and obtain the network equilibrium equation in matrix form using KCL.



oriented graph

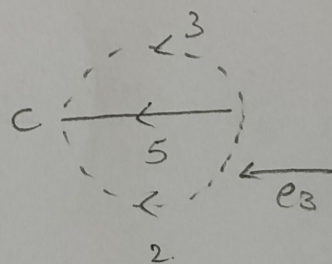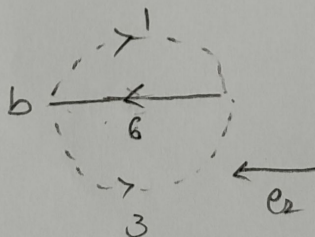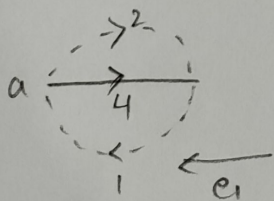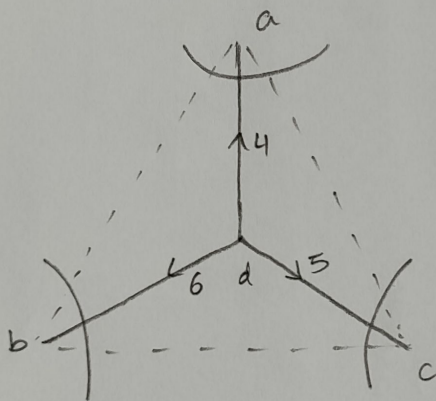

	Branches					
node voltages	1	2	3	4	5	6
$e_1(1,2,4)$	1	-1	0	1	0	0
$e_2(1,3,6)$	-1	0	-1	0	0	1
$e_3(2,3,5)$	0	1	1	0	1	0

Row wise $\rightarrow$ branch currents

$$j_1 - j_2 + j_4 = 0$$

$$-j_1 - j_3 + j_6 = 0$$

$$j_2 + j_3 + j_5 = 0$$

Column wise $\rightarrow$ branch voltages

$$v_1 = e_1 - e_2$$

$$v_2 = -e_1 + e_3$$

$$v_3 = -e_2 + e_3$$

$$v_4 = e_1$$

$$v_5 = e_3$$

$$v_6 = e_2$$

from the given circuit,

$$r_1 = 1 \Omega$$

$$r_4 = 2 \Omega$$

$$r_2 = 1 \Omega$$

$$r_5 = 2 \Omega$$

$$r_3 = 1 \Omega$$

$$r_6 = 2 \Omega$$

using ohm's law,

$$(V = IR)$$

$$V_1 = j_1 x_1 = 2 \Rightarrow j_1 - 2$$

$$V_2 = j_2 x_2 \Rightarrow j_2$$

$$V_3 = j_3 x_3 \Rightarrow j_3$$

$$V_4 = j_4 x_4 \Rightarrow 2j_4$$

$$V_5 = j_5 x_5 \Rightarrow 2j_5$$

$$V_6 = j_6 x_6 \Rightarrow 2j_6$$

Substitute eqn (3) in (2),

$$\circ j_1 - 2 = e_1 - e_2 = e_1 - e_2 + 2.$$

$$\circ j_2 = -e_1 + e_3$$

$$\circ j_3 = -e_2 + e_3$$

$$\circ j_4 = e_1 / 2$$

$$\circ 2j_5 = e_3 / 2$$

$$\circ 2j_6 = e_2 / 2$$

$$j_1 - j_2 + j_4 = 0$$

$$\circ e_1 - e_2 + 2 + e_1 + e_3 + e_1 / 2 = 0$$

$$2.5e_1 - e_2 + e_3 = -2 \rightarrow (a)$$

$$\circ -e_1 - e_2 + 2 + e_2 + e_3 + \frac{e_2}{2} = 0$$

$$-e_1 + 2.5e_2 - e_3 = 2 \rightarrow (b)$$

$$\circ -e_1 + e_3 + (-e_2 + e_3) + \frac{e_3}{2} = 0.$$

$$-e_1 - e_2 + 2.5e_3 = 0 \rightarrow (c)$$

Equations (a), (b) and (c) are termed as equilibrium equations.

In matrix form,




$$\begin{bmatrix} 2.5 & -1 & -1 \\ -1 & 2.5 & -1 \\ -1 & -1 & 2.5 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} -2 \\ 2 \\ 0 \end{bmatrix}$$

$$e_1 = -0.571 \text{ V}$$

$$e_2 = 0.57 \text{ V}$$

$$e_3 = 0$$

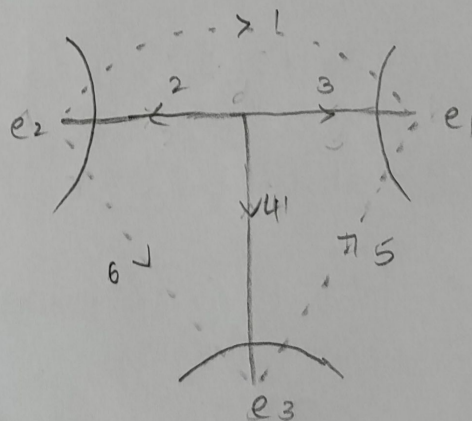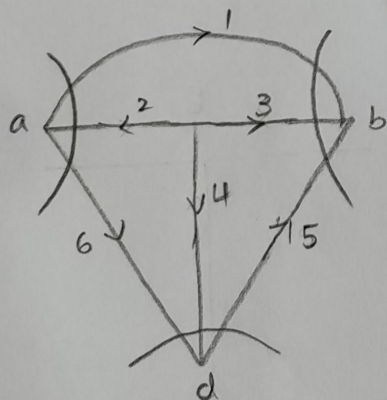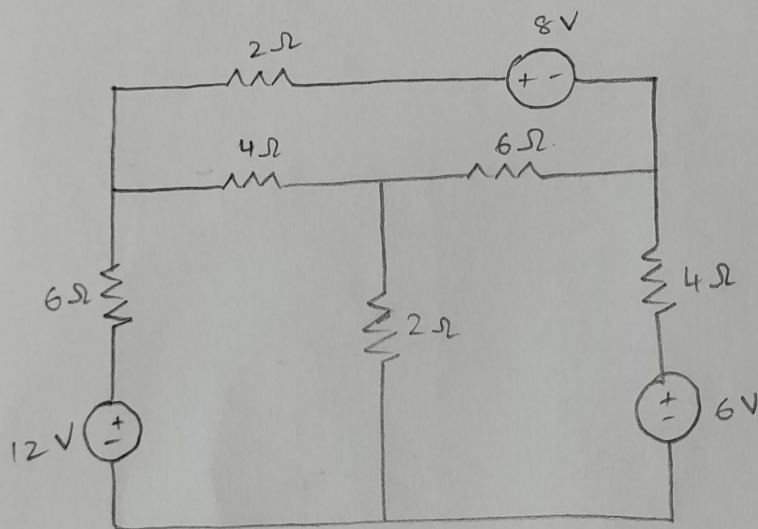4. For the network shown in Figure, write down the cutset matrix and obtain the network equilibrium equations.



	1	2	3	4	5	6
$e_1(1,3,5)$	1	0	1	0	1	0
$e_2(1,2,6)$	-1	1	0	0	0	-1
$e_3(4,5,6)$	0	0	0	1	-1	1

$$j_1 + j_3 + j_5 = 0$$

$$-j_1 + j_2 - j_6 = 0$$

$$j_4 - j_5 + j_6 = 0$$

$$v_1 = e_1 - e_2$$

$$v_2 = e_2$$

$$v_3 = e_1$$

$$v_4 = e_3$$

$$v_5 = e_1 - e_3$$

$$v_6 = -e_2 + e_3$$

$$v_1 = 2j_1 + 8$$

$$v_2 = 4j_2$$

$$v_3 = 6j_3$$

$$v_4 = 2j_4$$

$$v_5 = 4j_5 - 6$$

$$v_6 = 6j_6 + 12$$

$$j_1 = \frac{e_1 - e_2 - 8}{2}$$

$$j_2 = \frac{e_2}{4}$$

$$j_3 = \frac{e_1}{6}$$

$$j_4 = \frac{e_3}{2}$$

$$j_5 = \frac{e_1 - e_3 + 6}{4}$$

$$j_6 = \frac{-e_2 + e_3 - 12}{6}$$

substitute,

$$\frac{e_1 - e_2 - 8}{2} + \frac{e_1}{6} + \frac{e_1 - e_3 + 6}{4} = 0$$

$$0.91e_1 - 0.5e_2 - 0.25e_3 = 2.5 \rightarrow \textcircled{1}$$

$$-\left(\frac{e_1 - e_2 - 8}{2}\right) + \frac{e_2}{4} - \left[\frac{-e_2 + e_3 - 12}{6}\right] = 0$$

$$-0.5e_1 + 0.91e_2 - 0.16e_3 = -6 \rightarrow \textcircled{2}$$

$$0.5e_3 - \left(\frac{e_1 - e_3 + 6}{4}\right) + \left(\frac{-e_2 + e_3 - 12}{6}\right)$$

$$-0.25e_1 - 0.16e_2 + 0.91e_3 = 3.5 \rightarrow \textcircled{3}$$

$$e_1 = 0.277$$

$$e_2 = -5.93$$

$$e_3 = 2.87$$

$$V_1 = 6.207$$

$$V_2 = -5.93$$

$$V_3 = 0.277$$


$$V_4 = 2.87$$

$$V_5 = -2.59$$


$$V_6 = 8.8$$

6. Explain the following with respect to Network topology

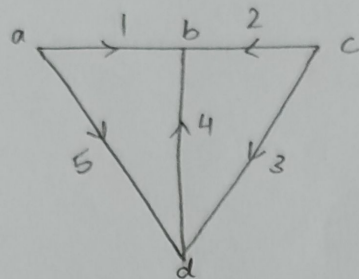i. Oriented graph - a graph is said to be oriented when all nodes are named, ~~all its~~ and arbitrary orientations are assigned to the branches which indicate the direction of branch currents.



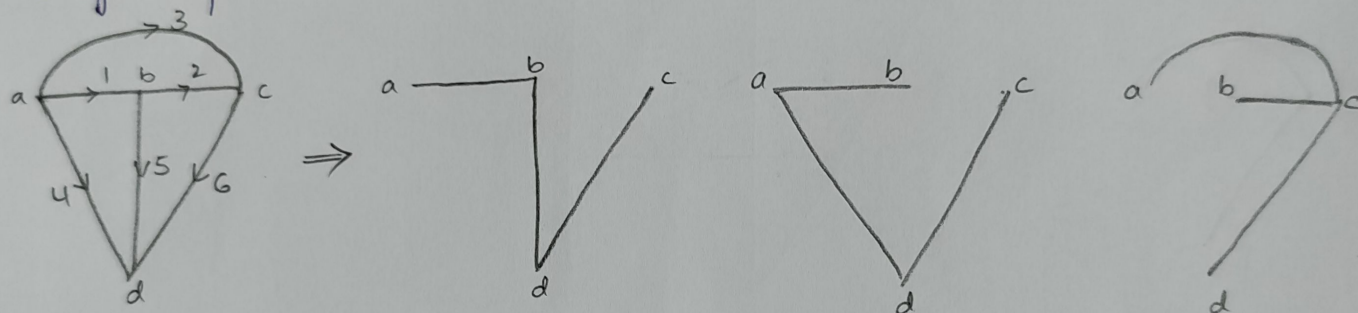ii. Tree - it is defined as a connected subgraph of a connected graph containing all the nodes of the graph but without any loops.




iii. Link - the branches which are not on the tree are termed as links or chords.

iv. Co-tree - The complement of tree is called co-tree which constitutes all the links.


v. Connected graph - If there exists at least one path from each node to every other node it is called connected graph.

7. Draw the oriented graph from the complete incidence matrix given below.

Nodes ↓		Branches →							
		1	2	3	4	5	6	7	8
1		1	0	0	0	1	0	0	1
2		0	1	0	0	-1	1	0	0
3		0	0	1	0	0	-1	1	-1
4		0	0	0	1	0	0	-1	0
5		-1	-1	-1	-1	0	0	0	0

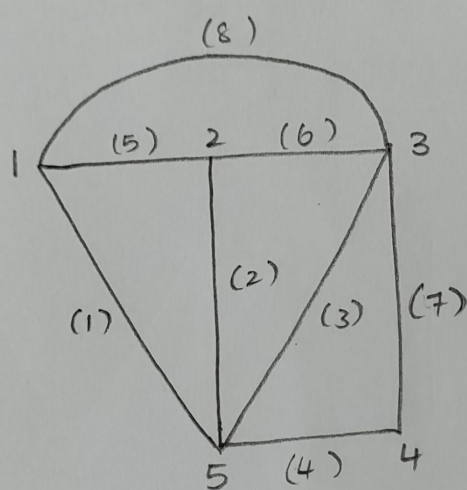

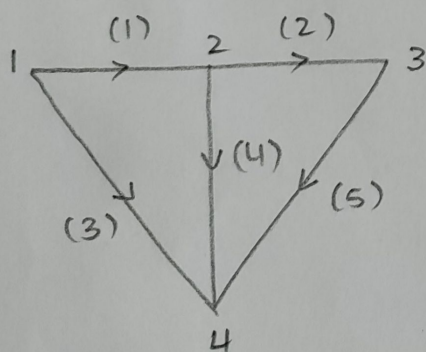8. Determine and draw the number of possible trees for the graph shown.



		(1)	(2)	(3)	(4)	(5)
1		1	0	1	0	0
2		-1	1	0	1	0
3		0	-1	0	0	1
4		0	0	-1	-1	-1

$$A_{ij} = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ -1 & 1 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & 1 \\ 0 & 0 & -1 & -1 & -1 \end{bmatrix} \leftarrow$$

$$A = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 \\ -1 & 1 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & 1 \end{bmatrix}_{3 \times 5}$$

$$A^T = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}_{5 \times 3}$$

$$A \cdot A^T = \begin{bmatrix} 2 & -1 & 0 \\ -1 & 3 & -1 \\ 0 & -1 & 2 \end{bmatrix} = 8$$

