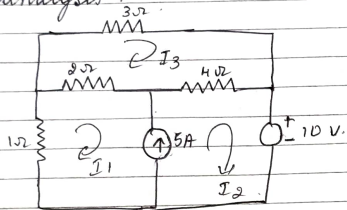



Module (01) :- Basic circuit analysis concepts

Unit 1 :-

- ① Determine the loop currents using Mesh analysis.



⇒ Mesh (01) and (02) forms supernode

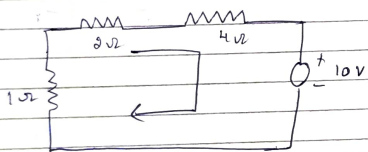

Applying KVL to supernode
 $-I_1 - 3(I_1 - I_3) - 4(I_2 - I_3) = 10$
 $-3I_1 - 4I_2 + 6I_3 = 10$ — ①

constraint eqn.

$$I_2 - I_1 = 5 \quad \text{--- ②}$$

Apply KVL to loop 3

$$-3I_3 - 4(I_3 - I_2) - 2(I_3 - I_1) = 0$$


$$+2I_1 + 4I_2 - 9I_3 = 0$$

$$-2I_1 - 4I_2 + 9I_3 = 0 \quad \text{--- ③}$$

Solving ①, ②, ③

$$I_1 = -5.5 \text{ A} \quad I_2 = -0.55 \text{ A} \quad I_3 = -1.48 \text{ A}$$

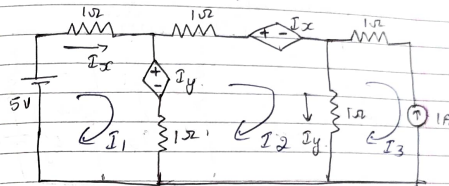- 2) Find the current in the three meshes for the figure shown.



$$\Rightarrow \begin{aligned} I_x &= I_1 \\ I_y &= I_2 - I_3 \end{aligned}$$

Apply KVL for mesh 01

$$5 - I_1 - I_y - 1(I_1 - I_2) = 0$$

$$5 - I_1 - I_y - I_1 + I_2 = 0$$

$$5 - I_1 - (I_2 - I_3) - I_1 + I_2 = 0$$

$$5 - I_1 - I_2 + I_3 - I_1 + I_2 = 0$$

$$-2I_1 + I_3 = -5 \quad \text{--- ①}$$

Apply KVL to mesh 02

$$-I_2 - I_x - 1(I_2 - I_3) - 1(I_2 - I_1) + I_y = 0$$

$$-I_2 - (I_1) - I_2 + I_3 - I_2 + I_1 + I_2 - I_3 = 0$$

$$-2I_2 = 0$$

$$I_2 = 0 \text{ A} \quad \text{--- ②}$$

From mesh 03

$$I_3 = 1 \text{ A}$$

substitute in ①


$$-2I_1 + I_3 = -5 \quad \Rightarrow -2I_1 + 1 = -5$$

$$-2I_1 + 1 = -5 \quad \Rightarrow -2I_1 = -6 \quad \Rightarrow I_1 = 3 \text{ A}$$

$$-2I_1 = -4$$

$$I_1 = 2A$$

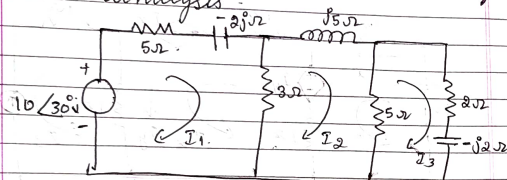③ Determine loop currents using mesh analysis.



⇒ Applying KVL to mesh (01).

$$10\angle 30^\circ - 5I_1 - 2jI_1 - 3(I_1 - I_2) = 0$$

$$10\angle 30^\circ - 5I_1 - 2jI_1 - 3I_1 + 3I_2 = 0$$

$$(-I_1)(8 + 2j) + 3I_2 = -10\angle 30^\circ$$

$$(8 + 2j)I_1 - 3I_2 = 10\angle 30^\circ \quad \text{--- (1)}$$

Applying KVL to mesh 02

$$-3(I_2 - I_1) - 5jI_2 - 5(I_2 - I_3) = 0$$

$$-3I_2 + 3I_1 - 5jI_2 - 5I_2 + 5I_3 = 0$$

$$+3I_1 - I_2(8 + j5) + 5I_3 = 0 \quad \text{--- (2)}$$

Applying KVL to mesh 03

$$-2I_3 - j2I_3 - 5(I_3 - I_2) = 0$$

$$-2I_3 - j2I_3 - 5I_3 + 5I_2 = 0$$

$$5I_2 - I_3(7 - j2) = 0$$

using Cramer's Rule.

$$\begin{bmatrix} 8 + j2 & -3 & 0 \\ -3 & 8 + j5 & -5 \\ 0 & -5 & 7 - j2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10\angle 30^\circ \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = (8 + j2) [(8 + j5)(7 - j2)] - (-5 \times -5) + 3 [(-3)(7 - j2)] + 0$$

$$\Delta = (8 + j2) [56 + 19j - 22] + 3(-21 + 6j)$$

$$= (8 + j2) [41 + 19j] - 63 + 18j$$

$$\Delta = 366 + 70j - 63 + 18j$$

$$\Delta = 303 + 18j = 315.52 \angle 16.19^\circ$$

$$\Delta_1 = \begin{bmatrix} 10\angle 30^\circ & -3 & 0 \\ 0 & 8 + j5 & -5 \\ 0 & -5 & 7 - j2 \end{bmatrix}$$

$$\Delta_1 = 10\angle 30^\circ [41 + 19j] + 3(0) + 0$$

$$\Delta_1 = 10\angle 30^\circ \times 45 \angle 24.86^\circ$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{10\angle 30^\circ \times 45 \angle 24.86^\circ}{315.52 \angle 16.19^\circ}$$

$$I_1 = 1.43 \angle 38.77^\circ A$$

$$\Delta_2 = \begin{bmatrix} 8 + j2 & 10\angle 30^\circ & 0 \\ -3 & 0 & -5 \\ 0 & 0 & 7 - j2 \end{bmatrix}$$

$$= 0 - 10\angle 30^\circ [-3(7 - j2)] + 0$$

$$= -10\angle 30^\circ [-21 + 6j]$$

$$\Delta_2 = -10\angle 30^\circ \times 21.84 \angle -15.95^\circ$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-10\angle 30^\circ \times 21.84 \angle -15.95^\circ}{315.52 \angle 16.19^\circ}$$

$$I_2 = 0.693 \angle -2.2^\circ A$$

$$\Delta_3 = \begin{bmatrix} 8.2^\circ & -3 & 10 \angle 30^\circ \\ -3 & 8+j5 & 0 \\ 0 & -5 & 0 \end{bmatrix}$$

$$\Delta_3 = 0 + 0 + 10 \angle 30^\circ [15 - 0]$$


$$= 150 \angle 30^\circ (15)$$

$$\Delta_3 = 150 \angle 30^\circ$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{150 \angle 30^\circ}{315.52 \angle 16.19^\circ}$$

$$I_3 = 0.476 \angle 13.8^\circ \text{ A}$$

4) Determine loop currents

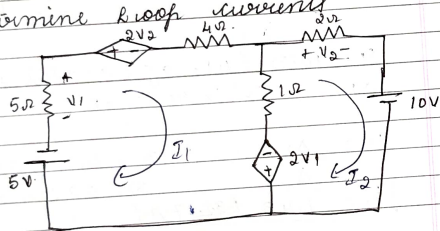

$$\Rightarrow V_1 = -5I_1$$

$$V_2 = 2I_2$$

Apply KVL to mesh 1.

$$-5 - 5I_1 - 2V_2 - 4I_1 - (I_1 - I_2) + 2V_1 = 0$$

$$-5 - 5I_1 - 2(2I_2) - 4I_1 - I_1 + I_2 + 2V_1 = 0$$

$$20I_1 + 3I_2 = -5 \quad \text{--- (1)}$$

Applying KVL to mesh 2.

$$-2V_1 - (I_2 - I_1) - 2I_2 - 10 = 0$$

$$-2(-5I_1) - I_2 + I_1 - 2I_2 = 10$$


$$11I_1 - 3I_2 = 10 \quad \text{--- (2)}$$

Solving (1) & (2)

$$I_1 = 0.161 \text{ A}$$

$$I_2 = -2.742 \text{ A}$$

Determine the loop currents

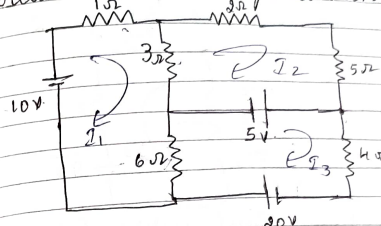

Apply KVL to mesh 1

$$10 - 1(I_1) - 3(I_1 - I_2) - 6(I_1 - I_3) = 0$$

$$10 - I_1 - 3I_1 + 3I_2 - 6I_1 + 6I_3 = 0$$

$$-10I_1 + 3I_2 + 6I_3 = -10$$

$$10I_1 - 3I_2 - 6I_3 = 10 \quad \text{--- (1)}$$

Apply KVL to mesh 2

$$-2I_2 - 5I_2 - 5 - 3(I_2 - I_1) = 0$$

$$-2I_2 - 5I_2 - 5 - 3I_2 + 3I_1 = 0$$

$$-3I_1 - 10I_2 = 5 \quad \text{--- (2)}$$

Apply KVL to mesh 3

$$+5 - 4I_3 + 20 - 6(I_3 - I_1) = 0$$

$$5 - 4I_3 + 20 - 6I_3 + 6I_1 = 0$$

$$6I_1 - 10I_3 + 25 = 0$$

$$-6I_1 + 10I_3 = 25 \quad \text{--- (3)}$$


Solving (1) (2) (3)

$$I_1 = 4.27 \text{ A}$$

$$I_2 = 0.79 \text{ A}$$

$$I_3 = 5.06 \text{ A}$$

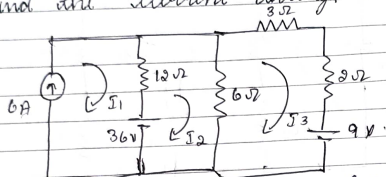- 6) Determine the loop currents and find the current through 3Ω resistor.



$\Rightarrow$ Mesh 1 contains current source of 6A
 $\therefore I_1 = 6A$

Apply KVL to mesh 02

$$36 - 12(I_2 - I_1) - 6(I_2 - I_3) = 0$$

$$36 - 12I_2 + 12I_1 - 6I_2 + 6I_3 = 0$$

$$36 - 18I_2 + 12(6) + 6I_3 = 0$$

$$-18I_2 + 6I_3 = -108$$

$$18I_2 - 6I_3 = 108 \quad \text{--- (1)}$$

Apply KVL to mesh 03

$$-3I_3 - 2I_3 - 9 - 6(I_3 - I_2) = 0$$


$$-3I_3 - 2I_3 - 9 - 6I_3 + 6I_2 = 0$$

$$6I_2 - 11I_3 = 9 \quad \text{--- (2)}$$

Solving (1) & (2)

$$I_2 = 3A \quad I_3 = 3A$$

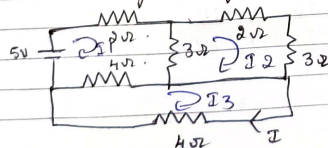- 7) Determine the loop currents using loop method of analysis



Apply KVL for mesh 01

$$5 - 2I_1 - 3(I_1 - I_2) - 4(I_1 - I_3) = 0$$

$$5 - 2I_1 - 3I_1 + 3I_2 - 4I_1 + 4I_3 = 0$$

$$-9I_1 + 3I_2 + 4I_3 = -5$$

$$4I_3 + 9I_1 - 3I_2 = +5 \quad \text{--- (1)}$$

Apply KVL to mesh 02

$$-3(I_2 - I_1) - 2I_2 - 3I_2 = 0$$

$$-3I_2 + 3I_1 - 2I_2 - 3I_2 = 0$$

$$-8I_2 + 3I_1 = 0$$

$$-3I_1 + 8I_2 = 0 \quad \text{--- (2)}$$

Apply KVL to mesh 03

$$-4(I_3 - I_1) - 4I_3 = 0$$

$$-4I_3 + 4I_1 - 4I_3 = 0$$

$$-4I_1 + 8I_3 = 0 \quad \text{--- (3)}$$

Apply KVL to mesh 01

$$5 - 2I_1 - 3(I_1 - I_2) - 4(I_1 - I_3) = 0$$

$$5 - 2I_1 - 3I_1 + 3I_2 - 4I_1 + 4I_3 = 0$$

$$-9I_1 + 3I_2 + 4I_3 = -5$$

$$9I_1 - 3I_2 - 4I_3 = 5 \quad \text{--- (3)}$$

$$I_1 = 0.851$$

$$I_2 = 0.319$$

$$I_3 = 0.425$$

- 8) Explain the classification of electrical network

The electrical networks are classified into

a) Unilateral (or) Bilateral

- (b) Linear (or) nonlinear
(c) Lumped (or) distributed
(d) Active (or) Passive

a) Unilateral (or) Bilateral n/w:-

Unilateral n/w is the one whose properties / characteristics ~~do not~~ change with direction of operation.

Eg: diode, rectifier

+ Bilateral n/w is the one whose properties / characteristics do not change / are same in either direction.

Eg: Resistance

b) Linear (or) nonlinear n/w:-

Linear n/w is the one whose parameters are constant i.e., they do not change with voltage (or) current & obeys law of superposition.

Eg: Mesh

Nonlinear n/w is the one whose properties / parameters change with voltage or current (It does not obey law of superposition).

Eg: electrical elements

c) Lumped (or) distributed:-

Lumped n/w is the one in which various electrical elements can

be separable physically and it is represented by ordinary differential eqn.

Eg: RLC

A distributed n/w is the one in which various electrical elements cannot be separated physically.

Eg: Power transmission lines

d) Active (or) Passive:-

Active n/w is the one in which consists of one (or) more emf source in it.

Eg: voltage source, current source

Passive n/w is the one in which contains no source of emf.

Eg: resistor, inductor

9) Explain with an example dependent independent sources and supermesh.


=> Independent Sources:-

opp characteristics of an independent source are not dependent on any n/w variable such as a current or voltage. It is of 2 types

1) Independent voltage source:- It is the one which is a two terminal n/w element that establishes a specified voltage across its terminals.



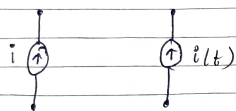
1) Independent current source: It is the one which is a two terminal n/w element which produces a specific current.




Dependent Sources:

If the voltage or current of a source depends in turn upon some other voltage or current it is called as dependent sources.

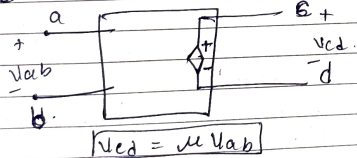a) Voltage Controlled Voltage Source (VCVS)
It is a four terminal n/w that establishes a voltage V_{cd} b/w two points c and d in the ckt. that is proportional to a voltage V_{ab} b/w a and b.




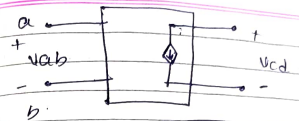b) Voltage Controlled Current Source (VCCS)
It is a four terminal n/w component that establishes current i_{cd} in a branch of the ckt that is proportional to the voltage V_{ab} b/w a and b.




$$i_{cd} = g_m V_{ab}$$

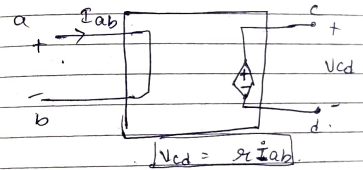
c) Current Controlled Voltage Source (CCVS)
It is a four terminal n/w component that establishes voltage V_{cd} b/w two points c and d in the ckt that is proportional to current I_{ab} in some branch of the ckt.



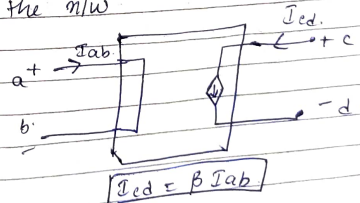
d) Current Controlled Current Source (CCCS)
It is the four terminal n/w component that establishes a current I_{cd} in one branch of a ckt that is proportional to the current I_{ab} in some branch of the n/w.



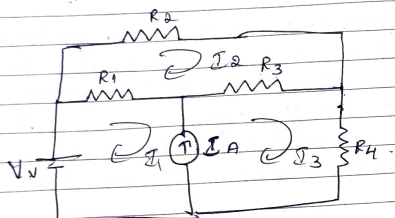Supernode: - Nodes that share a current source with other nodes, none of which contains a current source in the outer loop, form a supernode.



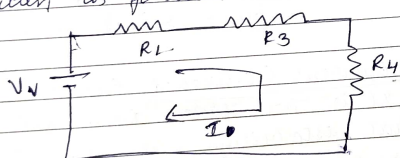In the above n/w I_1 & I_3 forms supernode and the n/w can be written as follows



The supernode eqⁿ can be written as


$$V_1 - R_1(I_1 - I_2) - R_3(I_3 - I_2) - R_4 I_3 = 0$$

 The constraint eqⁿ can be written as

$$I_3 - I_1 = I_2$$

Unit (Q2):-

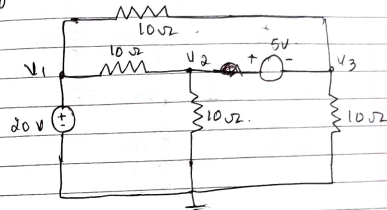① Apply nodal analysis to find node voltages V_1 , V_2 and V_3 .



$\Rightarrow$ Since V_1 is directly connected to 20V source $V_1 = 20V$

V_2 and V_3 forms supernode. Apply KCL to supernode

$$\frac{V_2 - V_1}{10} + \frac{V_2}{10} + \frac{V_3}{10} + \frac{V_3 - 20}{10} = 0$$

$$\frac{V_2 - 20}{10} + \frac{V_2}{10} + \frac{V_3}{10} + \frac{V_3 - 20}{10} = 0$$

$$(V_2 - 20) + V_2 + V_3 + (V_3 - 20) = 0$$

$$2V_2 + 2V_3 - 40 = 0$$

$$2V_2 + 2V_3 = 40$$

$$V_2 + V_3 = 20 \quad \text{--- (1)}$$

The voltage constraint eqⁿ is


$$V_2 - V_3 = 5 \quad \text{--- (2)}$$

Solving (1) & (2)

$$V_2 = 12.5V$$

$$V_3 = 7.5V$$

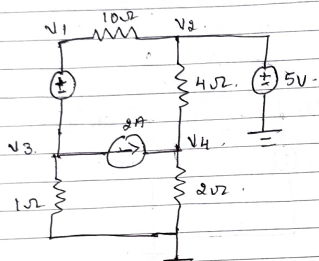- ③ For the circuit shown in figure determine all the node voltages.



=> node 1 and 3 form supernode.
constraint eqⁿ $V_1 - V_3 = 6$ — (1)

Apply KCL to ~~node~~ supernode.
 $\frac{V_1 - V_2}{10} + \frac{V_3}{1} + 2 = 0$

Since V_2 is directly connected to 5V source

$$V_2 = 5V$$

$$\frac{V_1 - 5}{10} + \frac{V_3}{1} + 2 = 0$$

$$0.1V_1 + V_3 = -1.5 \quad \text{--- (2)}$$

Apply KCL to node 4

$$\frac{V_4 - V_2}{4} + \frac{V_4}{2} = 2$$

$$0.75V_4 = 2 + \frac{V_2}{4}$$

$$0.75V_4 = 3.25$$

$$V_4 = \frac{3.25}{0.75}$$


$$V_4 = 4.33V$$

solving (1) & (2)

$$V_1 = 4.09V$$

$$V_3 = -1.90V$$

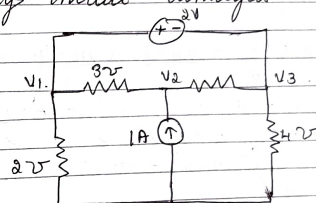- ④ Determine all the node voltages using nodal analysis



=> V_1 and V_3 form supernode.
constraint voltage eqⁿ

$$V_1 - V_3 = 2V \quad \text{--- (1)}$$

Apply KCL to ~~node~~ supernode
 $3(V_1 - V_2) + (V_1 - 0)2 + (V_3 - V_2)2 + (V_3 - 0)4 = 0$

$$3V_1 - 3V_2 + V_1 + 2 + 2V_3 - 2V_2 + 4V_3 = 0$$

$$5V_1 - 5V_2 + 6V_3 = 0 \quad \text{--- (2)}$$

Apply KCL to node 2

$$3(V_2 - V_1) + (V_2 - V_3)2 = 1$$

$$3V_2 - 3V_1 + 2V_2 - 2V_3 = 1$$

$$-3V_1 + 5V_2 - 2V_3 = 1 \quad \text{--- (3)}$$


solving (1) & (2) & (3)

$$V_1 = -1.16V$$

$$V_2 = -0.16V$$

$$V_3 = 0.83V$$

4) Find V_A and V_B .

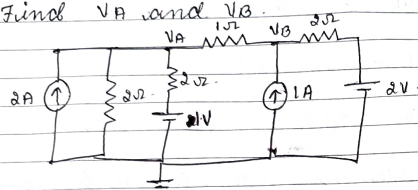

⇒ Apply KCR at node V_A .

$$-2 + \frac{V_A}{2} + \frac{V_A - 1}{2} + \frac{V_A - V_B}{1} = 0$$

$$-2 + V_A \left[\frac{1}{2} + \frac{1}{2} + 1 \right] - \frac{V_B - 1}{1} = 0$$

$$-5 + V_A(2) - V_B = 0$$

$$2V_A - V_B = 5/2$$

x by by 2 on B.S.

$$4V_A - 2V_B = 5 \quad \text{--- (1)}$$

Apply KCR to node V_B .

$$\frac{V_B - V_A}{1} + \frac{V_B - 2}{2} - 1 = 0$$

$$V_B(1 - 1/2) - V_A - 1 - 1 = 0$$

$$\frac{3V_B - V_A - 2}{2} = 0$$

x by by 2.


$$3V_B - V_A - 4 = 0$$

$$-2V_A + 3V_B = 4 \quad \text{--- (2)}$$

solving (1) & (2)

$$\boxed{V_A = 2.875V} \quad \boxed{V_B = 3.25V}$$

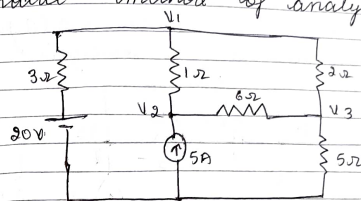5) Determine the node voltages using nodal method of analysis.



-1. Apply KCR at node 1.

$$\frac{V1 - V2}{1} + \frac{V1 - 20}{3} + \frac{V1 - V3}{2} = 0$$

$$\left(\frac{1}{3} + \frac{1}{2} + \frac{1}{2} \right) V1 - \frac{V2}{2} - \frac{V3}{2} - \frac{20}{3} = 0$$

$$1.83V1 - V2 - 0.5V3 = \frac{20}{3}$$

$$1.83V1 - V2 - 0.5V3 = 6.67 \quad \text{--- (1)}$$

Apply KCR at node 2.

$$\frac{V2 - V1}{1} + \frac{V2 - V3}{6} - 5 = 0$$

$$\left(\frac{1}{6} + \frac{1}{6} \right) V2 - \frac{V1}{1} - \frac{V3}{6} = 5$$

$$-V1 + 1.17V2 - 0.17V3 = 5 \quad \text{--- (2)}$$

Apply KCR at node 3.

$$\frac{V3 - V2}{6} + \frac{V3 - V1}{2} + \frac{V3}{5} = 0$$


$$\left(\frac{1}{6} + \frac{1}{2} + \frac{1}{5} \right) V3 - \frac{V2}{6} - \frac{V1}{2} = 0$$

$$-0.5V1 - 0.17V2 + 0.87V3 = 0 \quad \text{--- (3)}$$

solving (1), (2) & (3)

$$V_1 = 23.82 \text{ V} \quad V_2 = 27.4 \text{ V} \quad V_3 = 19.04 \text{ V}$$

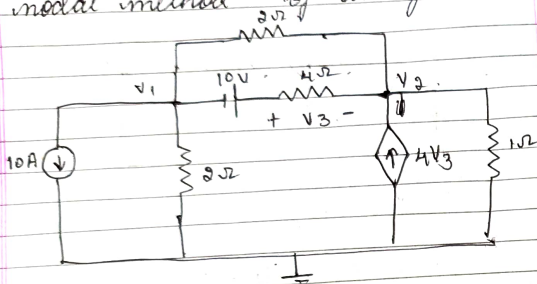⑥ Determine the node voltages using nodal method of analysis



⇒ Apply KCL to node 1:

$$10 + \frac{V_1}{2} + \frac{V_1 - V_2}{4} + \frac{V_1 + 10 - V_2}{4} = 0$$

$$\left(\frac{1}{2} + \frac{1}{4} + \frac{1}{4}\right)V_1 - \left(\frac{1}{4} + \frac{1}{4}\right)V_2 = -10 - 10$$

$$1.25V_1 - 0.75V_2 = -12.5 \quad \text{--- (1)}$$

Apply KCL to node 2:

$$\frac{V_2 - 10 - V_1}{4} + \frac{V_2 - V_1}{2} + \frac{V_2}{1} = 4V_3$$

$$\frac{V_2 - 10 - V_1}{4} + \frac{V_2 - V_1}{2} + \frac{V_2}{1} = 4(V_1 + 10 - V_2)$$

W.K.T

$$V_3 = V_1 - (-10) - V_2 = V_1 + 10 - V_2$$

$$\frac{V_2 - 10 - V_1}{4} + \frac{V_2 - V_1}{2} + \frac{V_2}{1} = 4(V_1 + 10 - V_2)$$

$$\frac{V_2 - 10 - V_1}{4} + \frac{V_2 - V_1}{2} + \frac{V_2}{1} - V_1 - 4 + 4V_2 = 40$$

$$V_2 \left(\frac{1}{4} + \frac{1}{2} + 1 + 4\right) - V_1 \left(\frac{1}{4} + \frac{1}{2} + 1\right) = 40 + 10$$


$$-4.75V_1 + 5.75V_2 = 42.5 \quad \text{--- (2)}$$

solving (1) & (2)

$$V_1 = -11.03 \text{ V}$$

$$V_2 = -1.72 \text{ V}$$

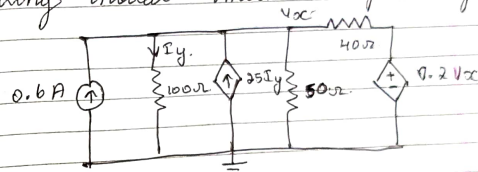⑦ Determine the node voltage V_x using nodal method of analysis



⇒ Apply KCL at node V_x :

$$\frac{V_x}{100} + \frac{V_x}{50} + \frac{V_x - 0.2V_x}{40} - 0.6 - 25I_y = 0$$

W.K.T

$$I_y = \frac{V_x}{100}$$


$$\frac{V_x}{100} + \frac{V_x}{50} + \frac{0.8V_x}{40} - 0.6 - 25\left(\frac{V_x}{100}\right) = 0$$

$$V_x \left(\frac{1}{100} + \frac{1}{50} + \frac{0.8}{40} - \frac{25}{100}\right) = 0.6$$

$$V_x(-0.2) = 0.6$$

$$V_x = -3 \text{ V}$$

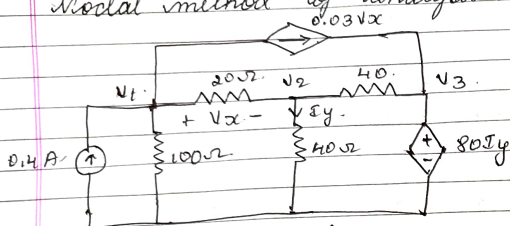- ③ Determine the node voltages using nodal method of analysis.



$\Rightarrow$ From the ckt -
 $V_x = V_1 - V_2$

$$I_y = \frac{V_2}{40}$$

Apply KCL to node 1.

$$\frac{V_1}{100} + \frac{V_1 - V_2}{20} + 0.03V_x - 0.4 = 0$$

$$\frac{V_1}{100} + \frac{V_1 - V_2}{20} + 0.03(V_1 - V_2) - 0.4 = 0$$

$$V_1 \left(\frac{1}{100} + \frac{1}{20} + 0.03 \right) - \left(\frac{1}{20} + 0.03 \right) V_2 = 0.4$$

$$0.09V_1 - 0.08V_2 = 0.4 \quad \text{--- (1)}$$

Apply KCL to node 2

$$\frac{V_2 - V_1}{20} + \frac{V_2 - V_3}{40} + \frac{V_2}{40} = 0$$

$$V_2 \left(\frac{1}{20} + \frac{1}{40} + \frac{1}{40} \right) - \frac{V_1}{20} - \frac{V_3}{40} = 0$$

$$-0.05V_1 + 0.1V_2 - 0.025V_3 = 0 \quad \text{--- (2)}$$

Apply KCL at node 3
~~Since~~ Since V_3 is directly connected to 80V source

$$V_3 = 80V$$

$$V_3 = 80 \left(\frac{V_2}{40} \right)$$

$$V_3 = 2V_2$$

$$2V_2 - V_3 = 0 \quad \text{--- (3)}$$

Solving (1) (2) (3).

$$V_1 = 40V$$





$$V_2 = 40V$$

$$V_3 = 80V$$

Network Analysis

Module 1 Unit 3

1) Find V_0 using source transformation?

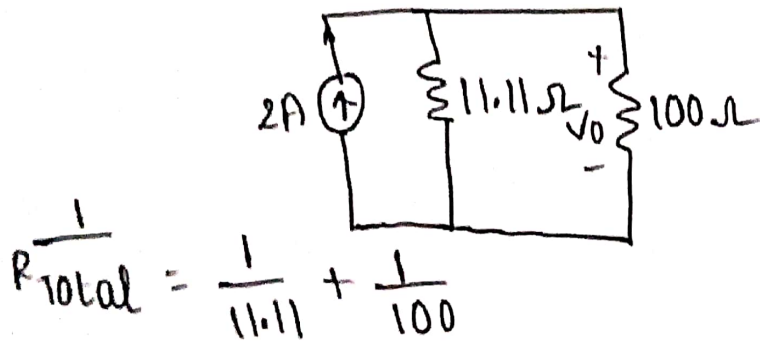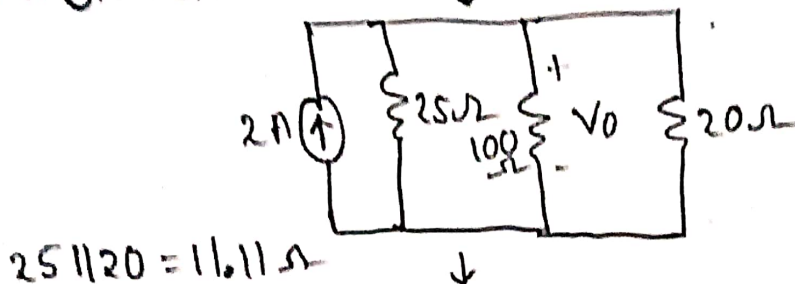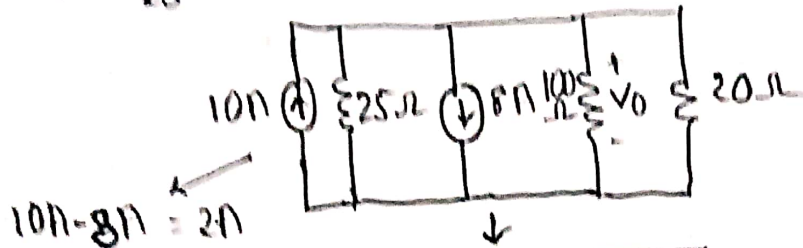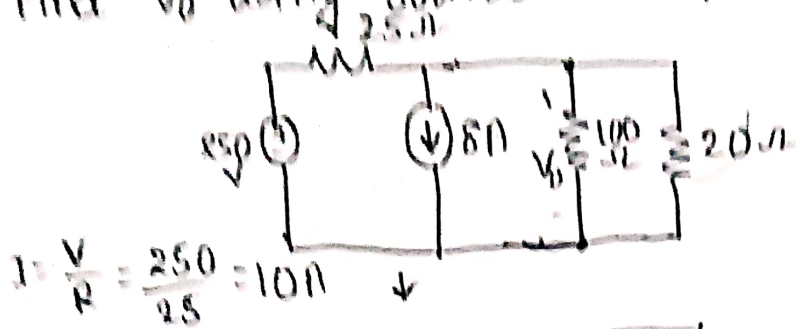


$$R_{total} = 10\Omega$$

$$V_0 = I_{net} \times R_{total}$$

$$= 2 \times 10\Omega = 20V$$

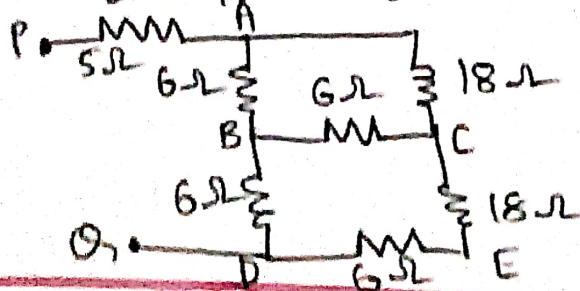2) Determine the input resistance between PQ using star-delta transformation.



ABC forms a closed delta loop.

$$R_{AB} = 6\Omega$$

$$R_{BC} = 6\Omega$$

$$R_{AC} = 18\Omega$$

By formulae



$$R_{AB} = \frac{R_{AB}}{R_A + R_B + R_C} \text{ \& others}$$

$$R_{sum} = R_{AB} + R_{BC} + R_{AC} = 6 + 6 + 18 = 30\Omega$$

$$R_A = \frac{R_{AB} \times R_{AC}}{sum} = \frac{6 \times 18}{30} = 3.6\Omega$$

$$R_B = \frac{R_{AB} \times R_{BC}}{sum} = \frac{6 \times 6}{30} = 1.2\Omega$$
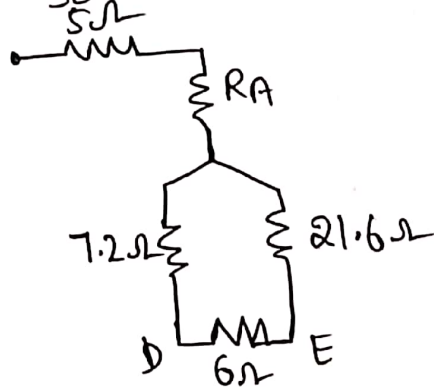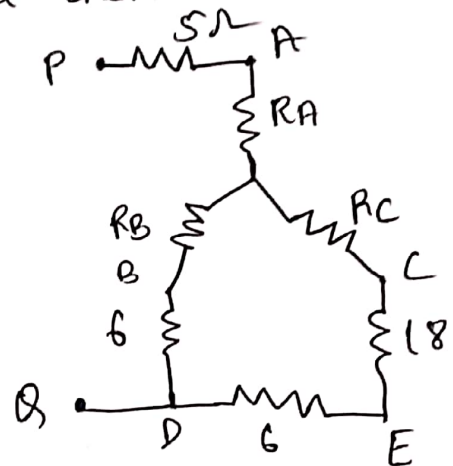
$$R_C = \frac{R_{BC} \times R_{AC}}{sum} = \frac{6 \times 18}{30} = 3.6\Omega$$




$$R_{DNE} = R_{left} + R_{right} = 7.2 + 21.6 = 28.8\Omega$$

$$R_{DE} = \frac{28.8 \times 6}{28.8 + 6} = \frac{172.8}{34.8} = 4.965\Omega$$

$$R_{PB} = 5\Omega + R_A + R_{DE} = 5 + 3.6 + 4.965 = 13.56\Omega$$

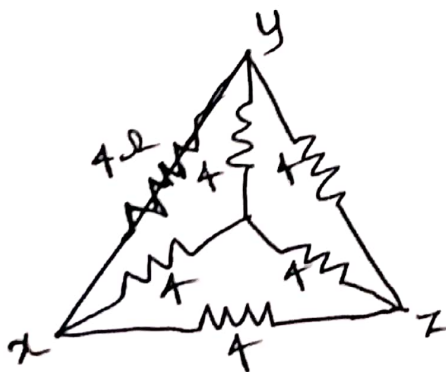③ For the Ckt shown in fig. Determine equivalent resistance between any 2 terminals



2 n/w $\rightarrow$ outer delta n/w
inner star n/w

convert inner star n/w to delta

$$R_x = 4\Omega, R_y = 4\Omega, R_z = 4\Omega$$

$$R_A = R_y + R_z + \frac{R_y R_z}{R_x} = 12$$



$$R_B = 12$$

$$R_C = 12 \text{ } \} \text{ similarly}$$

Now inner delta branch containing 12Ω at 3 sides is in parallel with outer delta branch containing 4Ω

$$\therefore R_p = \frac{4 \times 12}{4 + 12} = \frac{48}{16} = 3\Omega$$

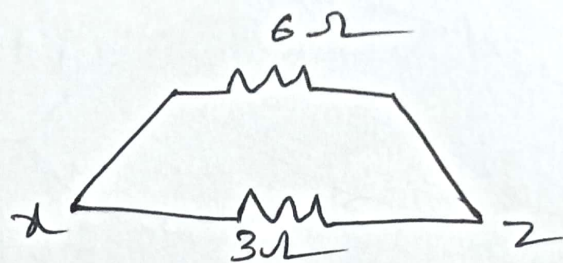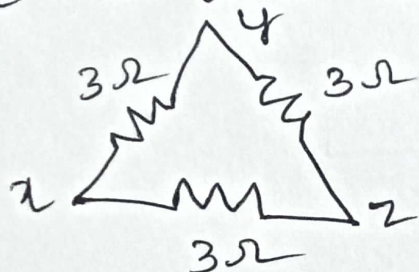entire ckt is simplified with 3Ω on each side a delta loop




Now $x-y$ & $y-z$ are in series by last n/w

$$6 \parallel 3 = \frac{3 \times 6}{3 + 6} = \frac{18}{9} = 2\Omega$$

$$R_{eq} = 2\Omega$$

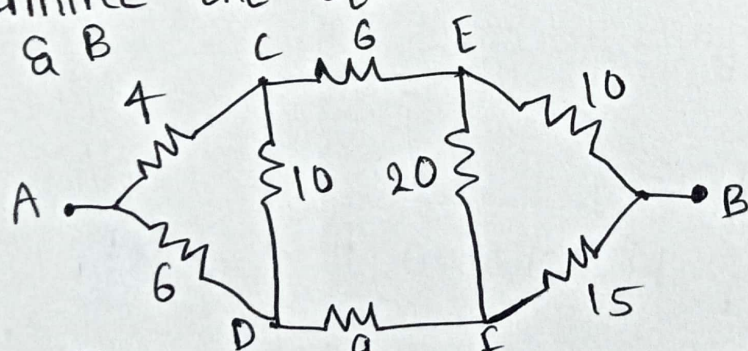④ Determine the equivalent resistance between terminals A & B



converting left delta n/w into star n/w

$$R_{AC} = 4\Omega$$

$$R_{AD} = 6\Omega$$

$$R_{CD} = 10\Omega$$

$$\text{sum} = 20\Omega$$

$$R_A = \frac{4 \times 6}{4 + 6 + 10} = \frac{24}{20} = 1.2\Omega$$

$$R_B = \frac{4 \times 10}{20} = \frac{40}{20} = 2\Omega$$

$$R_D = \frac{6 \times 10}{20} = \frac{60}{20} = 3\Omega$$

converting right delta n/w into star

$$\text{sum} = 10 + 15 + 20 = 45 \Omega$$

$$R_{EB} = 10 \Omega$$





$$R_{FB} = 15 \Omega$$

$$R_{EF} = 20 \Omega$$

$$R_B = \frac{10 \times 15}{45} = \frac{150}{45} = 3.33 \Omega$$


$$R_E = \frac{10 \times 20}{45} = 4.44 \Omega$$
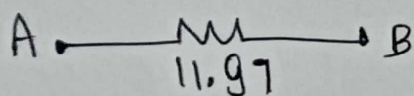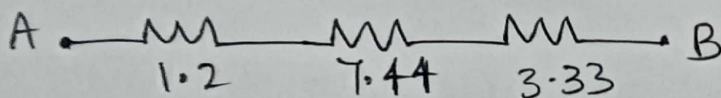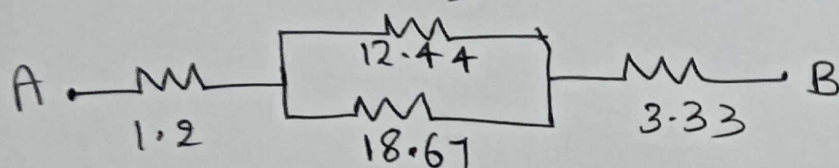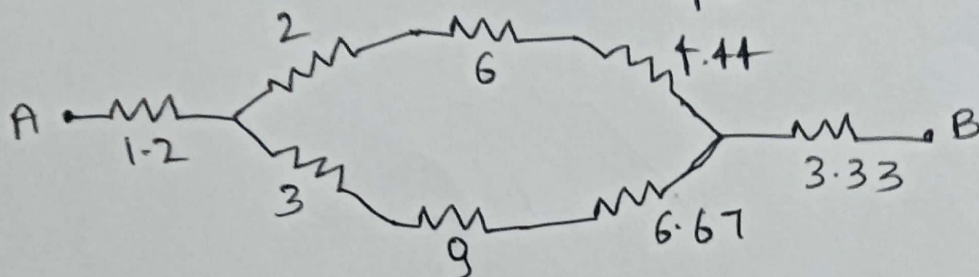
$$R_F = \frac{15 \times 20}{45} = 6.67 \Omega$$



$$R_{AB} = 11.97 \approx 12 \Omega$$

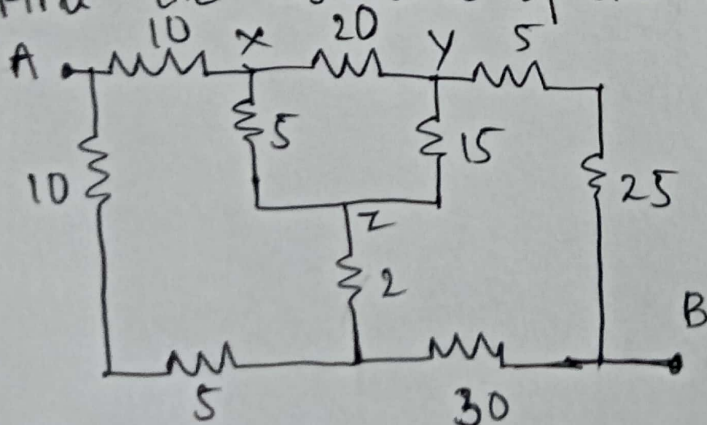⑤ Find the resistance of ckt shown b/w A & B



$$R_x = \frac{R_{xy} \times R_{xz}}{\text{sum}} = \frac{20 \times 5}{40} = 2.5 \Omega$$

$$R_y = \frac{R_{xy} \times R_{yz}}{\text{sum}} = \frac{20 \times 15}{40} = 7.5 \Omega$$


$$R_z = \frac{R_{xz} \times R_{yz}}{\text{sum}} = \frac{5 \times 15}{40} = 1.875 \Omega$$


$$R_{xy} = 20 \Omega$$

$$R_{xz} = 5 \Omega$$

$$R_{yz} = 15 \Omega$$

$$\text{sum} = 20 + 5 + 15 = 40 \Omega$$

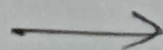


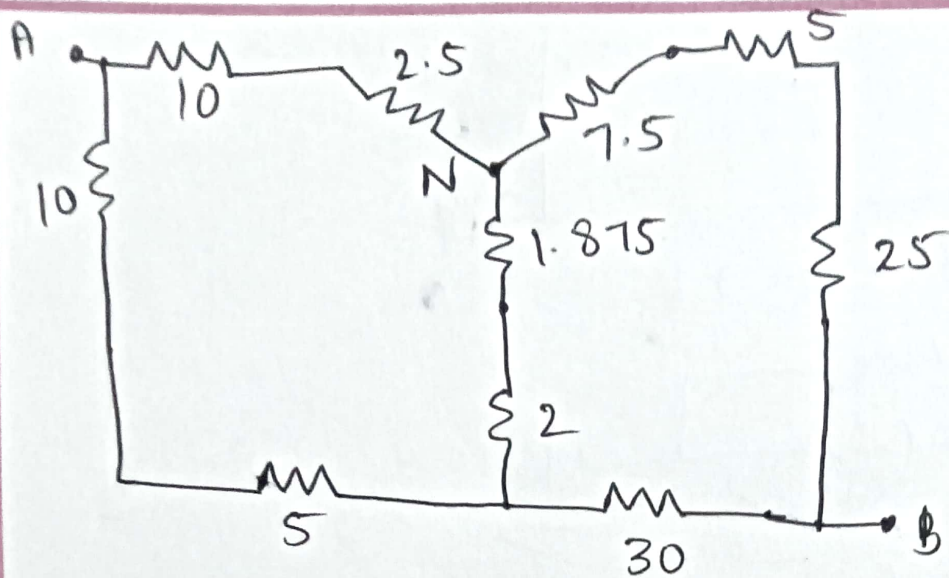

Now $\rightarrow 10 + 2.5 = 12.5\Omega \rightarrow R_{\text{branch-x}}$

$R_{\text{branch-y}} \rightarrow 30 + 7.5 = 37.5\Omega$

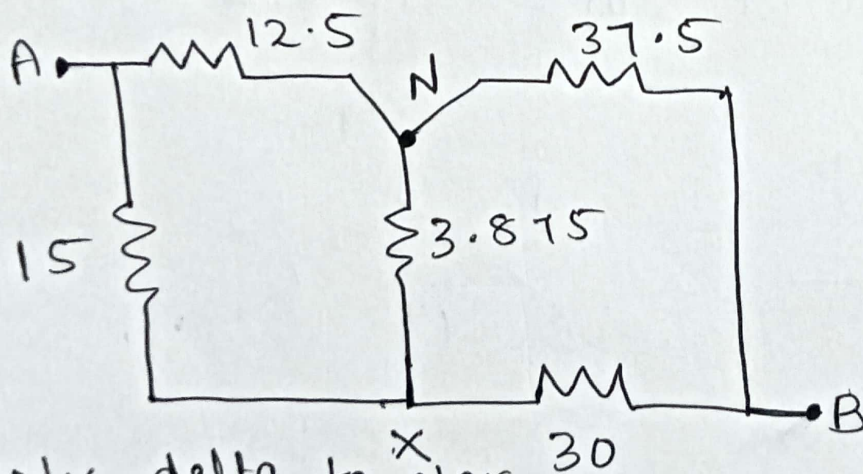$R_{\text{branch-z}} \rightarrow 1.875 + 2 = 3.875\Omega$







ANx - delta to star



$$R_1 = \frac{12.5 \times 3.875}{31.37} = 1.54\Omega$$

$$R_2 = \frac{12.5 \times 15}{31.37} = 5.97\Omega$$
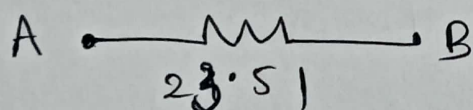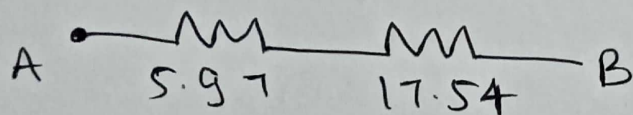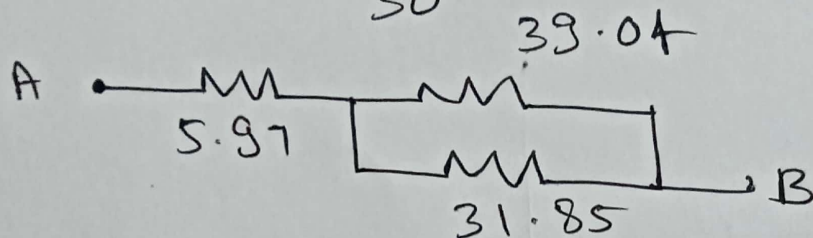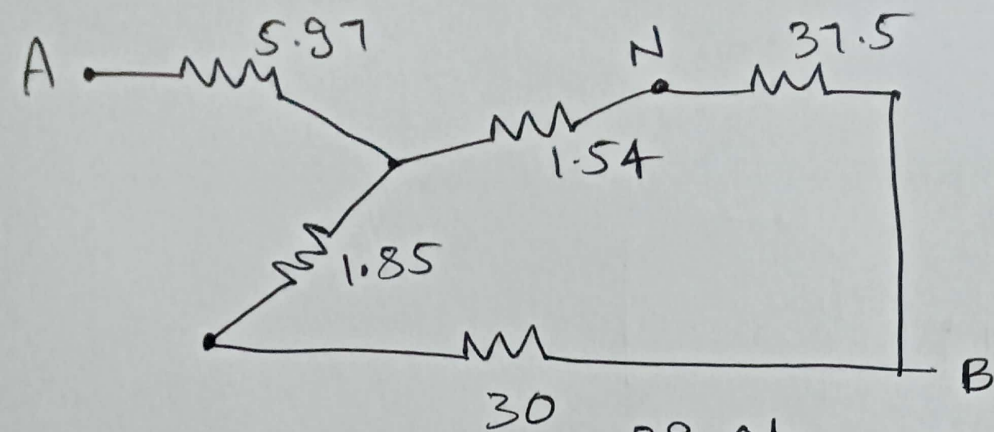
$$R_3 = \frac{3.875 \times 15}{31.37} = 1.85$$



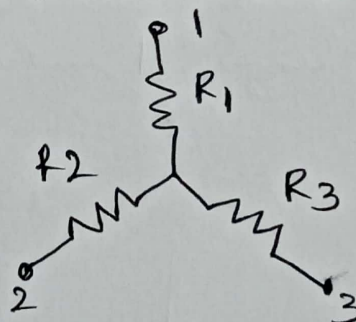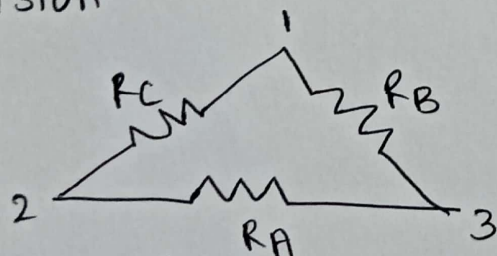⑥ obtain the expression for star to delta and delta to star conversion



Delta to star Transformation

$$\text{From terminal 1 \& 2} = R_C \parallel (R_A + R_B) = \frac{R_C(R_A + R_B)}{R_C + R_A + R_B}$$

Referring to star n/w shown the resistance b/w 1 & 2 = $R_1 + R_2$.

Since 2 n/w are electrically equivalent

$$R_1 + R_2 = \frac{R_C(R_A + R_B)}{R_A + R_B + R_C} \quad \text{--- (1)}$$

$$\& R_3 + R_1 = \frac{R_B(R_A + R_C)}{R_A + R_B + R_C} \quad \text{--- (3)}$$

similarly,

$$R_2 + R_3 = \frac{R_A(R_B + R_C)}{R_A + R_B + R_C} \quad \text{--- (2)}$$

subtracting ② & ①

$$R_1 - R_3 = \frac{R_B R_C - R_A R_B}{R_A + R_B + R_C} \quad \text{--- (4)}$$

Add ④ & ③

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C}$$

Similarly,

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$$

Thus, star resistor connected to a terminal is equal to product of 2 delta networks connected to same terminal divided by sum of delta resistors.

star to delta Transformation.

multiplying above eq

$$R_1 R_2 = \frac{R_A R_B R_C^2}{(R_A + R_B + R_C)^2} \quad \text{--- (5)}$$

$$R_2 R_3 = \frac{R_A^2 R_B R_C}{(R_A + R_B + R_C)^2} \quad \text{--- (6)}$$

$$R_3 R_1 = \frac{R_A R_B^2 R_C}{(R_A + R_B + R_C)^2} \quad \text{--- (7)}$$

Add ⑤, ⑥, ⑦

$$R_1 R_2 + R_2 R_3 + R_3 R_1$$

$$= \frac{R_A R_B R_C (R_A + R_B + R_C)}{(R_A + R_B + R_C)^2} = \frac{R_A R_B R_C}{R_A + R_B + R_C}$$

$$= R_A R_1 = R_B R_2 = R_C R_3$$


Hence,

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = R_1 + R_3 + \frac{R_3 R_1}{R_2}$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

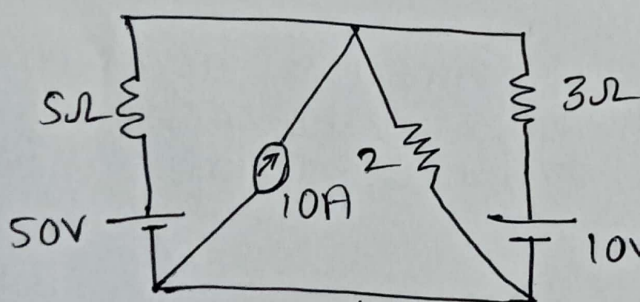⑦ Determine power delivered by 50V source using source transformation




$$V = IR$$

$$I = \frac{V}{R}$$


$$= \frac{10}{3}$$

$$= 3.33 \text{ A}$$

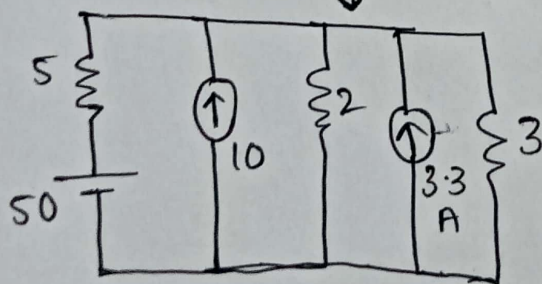


$$2\Omega \parallel 3\Omega = 1.2\Omega$$

$$10 + 3.3 = 13.3 \text{ A}$$

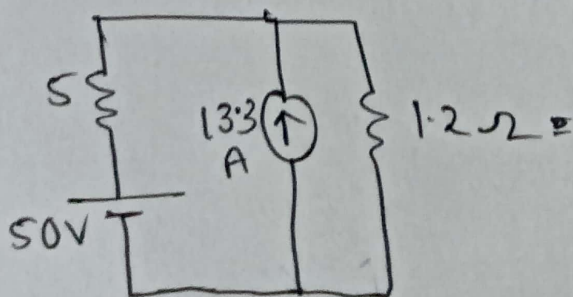



By source Transformation:

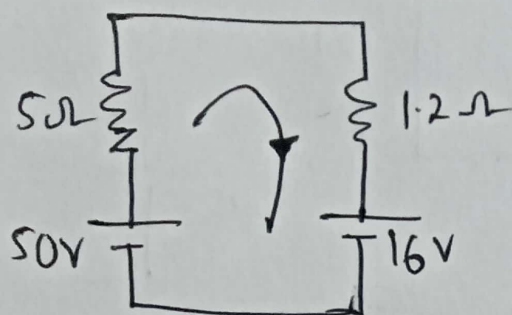

$$I = \frac{50 - 16}{5 + 1.2} = 5.48 \text{ A}$$

$$\text{Power} = 50 \times 5.48 = 274 \text{ W}$$

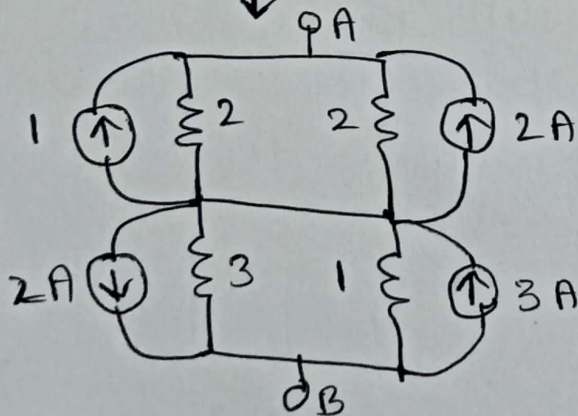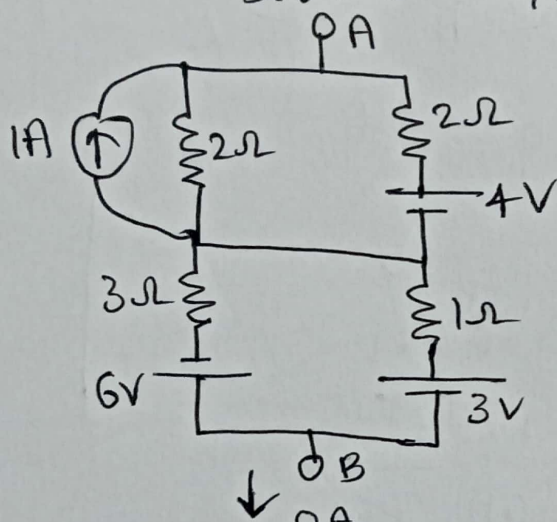8) Reduce the n/w shown in to a single source n/w



converting current sources into equivalent voltage sources

